

Mid Examination -Electrical and Electronics Measurements

u19ee015@eed.svnit.ac.in [Switch account](#)

 Draft saved

Your email will be recorded when you submit this form

* Required

Accuracy of rectifier type instruments is waveform dependent because... 1 point

- ☒ (a) form factor is waveform dependent
- ☐ (b) form factor is independent of waveform
- ☐ (c) form factor of rectifier element is waveform dependent
- ☐ (d) form factor is sometimes waveform dependent

Clear selection

In basic emitter follower voltmeter the voltage gain is .. 1 point

- ☐ (a) adjustable by adjusting emitter resistance
- ☐ (b) adjustable by adjusting excitation voltage
- ☒ (c) approximately unity only
- ☐ (d) dependent on base emitter junction voltage drop

Clear selection



The most economical RMS responding electronic voltmeter can be designed using..

1 point

- ☐ (a) nonlinear behavior of PN junction diode
- ☐ (b) linear behavior of Sampling register
- ☐ (c) linear behavior of electrostatic instrument
- ☐ (d) nonlinear behavior of inductor coil

Quasi RMS detector utilizes

1 point

- ☐ (a) Peak detector and average detector together
- ☐ (b) peak detector only
- ☐ (c) average detector only
- ☐ (d) temperature detector

Normally analogue instruments are designed for slightly less than the critical damping in order that

1 point

- ☐ (a) pointer reaches final deflection slowly.
- ☐ (b) pointer reaches final deflection without oscillations
- ☐ (c) pointer reaches final deflection and come to zero immediately
- ☐ (d) pointer reaches final deflection quickly even under elevated ambient temperature



The arm of a four arm bridge a,b,c,d supplied with sinusoidal voltage, have 1 point
the following values: arm ab: A resistance of 200 ohm in parallel with a
capacitance 1 uF, arm bc: 400 ohm resistance, arm cd: 1000 ohm
resistance, arm da: A resistance R2 in series with a 2 uF capacitance.
Determine the value of R2?

- ☐ (a) 1000 ohm
- ☐ (b) 600 ohm
- ☐ (c) 400 ohm
- ☒ (d) 398 ohm

Clear selection

A 1 mA Ammeter has a resistance of 100 Ω . It is to be converted to a 10A 1 point
ammeter. The value of shunt resistance required is ...

- ☐ (a) 0.1 Ω
- ☒ (b) 0.01 Ω
- ☐ (c) 0.001 Ω
- ☐ (d) 1.0 Ω

Clear selection



In electrodynamic wattmeter, the error due to pressure coil inductance increases with..

1 point

- ☐ (a)increase in humidity
- ☒ (b)increase in frequency
- ☐ (c)increase in atmospheric pressure
- ☐ (d)decrease in frequency

Clear selection

Which of the following method takes help of wheatstone bridge for measuring high resistance

1 point

- ☐ (a)Direct Deflection Method
- ☐ (b)Loss of Charge Method
- ☐ (c)Megger circuit
- ☒ (d)Mega Ohm Bridge Method

Clear selection

In which of the following bridge, the shielding is difficult

1 point

- ☒ (a) Aderson's Bridge
- ☐ (b) Maxwell's inductance Bridge
- ☐ (c) Hay's Bridge
- ☐ (d) Owen's Bridge

Clear selection

A bridge circuit works at a frequency of 2kHz. The following can be used as 1 point detectors for detection of null conditions in the bridge

- ☐ (a) Vibration galvanometer and headphones
- ☐ (b) Headphones and tunable amplifiers
- ☐ (c) Vibration galvanometer and tunable amplifiers
- ☒ (d) Vibration galvanometer, headphones and tunable amplifiers

Clear selection

When the localizing ground fault with the help of loop tests, the resistance 1 point of the fault:

- ☐ (a) affects the balance conditions
- ☒ (b) affects the value of cable resistance
- ☐ (c) affects the sensitivity of the bridge
- ☐ (d) all the above

Clear selection

If the resistance R_x is very large, then time for an appreciable fall in voltage 1 point (V) is _____in Loss of charge method.

- ☐ (a) Small
- ☐ (b) zero
- ☒ (c) large
- ☐ (d) None of the above

Clear selection



Admission No. *

U19EE015

A four arm ac bridge a,b,c,d has the following impedances Arm ab: $Z_1 = 200 \angle 60^\circ \Omega$ Arm ad: $Z_2 = 400 \angle 0^\circ \Omega$ Arm bc: $Z_3 = 300 \angle 0^\circ \Omega$ Arm cd: $Z_4 = 600 \angle 60^\circ \Omega$ Is it possible to balance the bridge under above conditions??

1 point

- ☐ YES
- ☒ NO

Clear selection

True RMS reading voltmeter uses two thermocouples in order ...

1 point

- ☐ (a) to increase measurement sensitivity
- ☐ (b) that it acts as averaging between two measurement instances
- ☐ (c) that it acts as averaging between two measurements spots
- ☒ (d) compensate for nonlinear behavior of measuring thermocouple

Clear selection



Wagner's Earth Device are used in a.c bridge circuits for;

1 point

- ☒ (a) Eliminating the effect of earth capacitances
- ☐ (b) Eliminating the effect of inter-component capacitances
- ☐ (c) Eliminating the effect of stray electrostatic fields
- ☐ (d) Shielding the bridge elements

Clear selection

In VHF oscilloscope where sampling technique is employed..

1 point

- ☐ (a) single shot phenomena can never be displayed
- ☐ (b) single shot phenomena can be displayed easily
- ☐ (c) single shot phenomena can be displayed occasionally
- ☐ (d) Single shot phenomena can be displayed if the delay line is shorted

In varley loop test the faulty and sound cables are identical with 0.4 ohm/km. The ratio arms are set at 25 ohm and 30 ohm. The values of variable resistance connected to faulty cable are 15 ohm and 10 ohm at 2 positions of the switch. Determine the length of each cable ??

1 point

- ☐ (a) 12.5 km
- ☐ (b) 6.25 km
- ☐ (c) 15.625 km
- ☒ (d) 5.682 km

Clear selection



In varley loop test the faulty and sound cables are identical with 0.4 ohm/km. The ratio arms are set at 25 ohm and 30 ohm. The values of variable resistance connected to faulty cable are 15 ohm and 10 ohm at 2 positions of the switch. Determine Fault Distance from test end ?? 1 point

- ☐ (a) 5.682 km
- ☐ (b) 12.5 km
- ☒ (c) 6.25 km
- ☐ (d) 15.625 km

Clear selection

In D'Sauty's bridge (unmodified form) it is: 1 point

- ☐ (a) Possible to obtain balance even if both the capacitors are imperfect
- ☐ (b) Possible to obtain balance if one of the capacitors are perfect
- ☒ (c) Possible to obtain the balance only if both the capacitors are perfect
- ☐ (d) All the above

Clear selection

What is the condition for maximum sensitivity of wheatstone bridge ? 1 point

- ☒ (a) $P/(P+Q) = R/(R+S)$
- ☐ (b) $R=S$
- ☐ (c) $R=0$
- ☐ (d) $S=0$

Clear selection



Balancing weights are added to the moving system in order to bring...

1 point

- ☐ (a) weight of the moving system to optimum level
- ☒ (b) center of gravity of moving system on axis of rotation
- ☐ (c) center of gravity of moving system away from axis of rotation
- ☐ (d) weight of the moving system to maximum level

Clear selection

The equations under balance conditions for bridge are: $R_1 = [(R_2 R_3)/R_4] - [r_1]$ 1 point
and $L_1 = (CR_3/R_4) [r(R_2 + R_4) + R_2 R_4]$, Where R_1 and L_1 are respectively unknown resistance and inductance. In order to achieve converging balance

- ☐ (a) R_2 and R_4 should be chosen as variables
- ☒ (b) r and r_1 should be chosen as variables
- ☐ (c) R_2 and r_1 should be chosen as variables
- ☐ (d) r and R_4 should be chosen as variables

Clear selection

The supply voltage (E) in maxwell's inductance and capacitance bridge is lead by an angle (α) with 1 point

- ☐ (a) I_c
- ☐ (b) I_2
- ☐ (c) E_2
- ☐ (d) I_1



Why we always rotate the generator handle at high speed in Megger

1 point

- ☐ (a) To avoid the error in measurement
- ☐ (b) To generate constant voltage
- ☐ (c) Both A&B
- ☐ (d) None of the above

Student 's Name *

Your answer

High torque to weight ratio is desirable in analogue indicating instruments to ensure ... 1 point

- ☐ (a) high friction loss
- ☒ (b) low friction loss
- ☐ (c) low hysteresis loss
- ☐ (d) high hysteresis loss

Clear selection



In wattmeter for high load current, pressure coil is connected to the load side since... 1 point

- ☐ (a) power loss in current coil is large compared to that in pressure coil
- ☐ (b) power loss in pressure coil is large compared to power consumed by the load
- ☐ (c) it is convenient for connections
- ☐ (d) power loss in pressure coil is small compared to power consumed by load

The accuracy of RMS responding voltmeter for measuring highly nonlinear waveform is limited by 1 point

- ☐ (a) input impedance of amplifiers
- ☐ (b) input capacitance of amplifiers
- ☐ (c) transconductance of amplifiers
- ☐ (d) the bandwidth of the amplifiers

A 35 Mhz oscilloscope has a displayed rise time of 18 nsec then signal rise time will be.. 1 point

- ☐ (a) 50 nsec
- ☐ (b) 15 nsec
- ☐ (c) 9 nsec
- ☐ (d) 35 nsec



In compensated wattmeter current passing through compensating coil is... 1 point

- ☐ (a)equal to current coil current
- ☐ (b)equal to 100 μ A
- ☐ (c)equal to pressure coil current
- ☐ (d)equal to load current

Submit

Clear form

Never submit passwords through Google Forms.

This form was created inside of Sardar Vallabhbhai National Institute of Technology, Surat. [Report Abuse](#)

Google Forms

